

寄存器传输级（RTL）设计方法

寄存器传输级设计方法

➤ 用寄存器保存中间数据


- 寄存器用于通用存储，就像算法中的变量

➤ 用专用的数据通路 (data path) 实现运算


- 数据处理电路
- 连接网络
- 寄存器

➤ 用专用的控制通路 (control path) 规定运算的顺序

- 状态机
- 在什么时间完成什么运算

 

Levels of digital design abstraction

 

Appropriate building blocks:

Tires, seat, pedals

Not:

Rubber, glue, metal

寄存器传输级设计方法


Step1: 算法和高层次状态机


Step2: 产生数据通路

Step3: 连接数据通路和控制器

Step4: 产生控制器状态机

Step 3: 连接数据通路和控制器

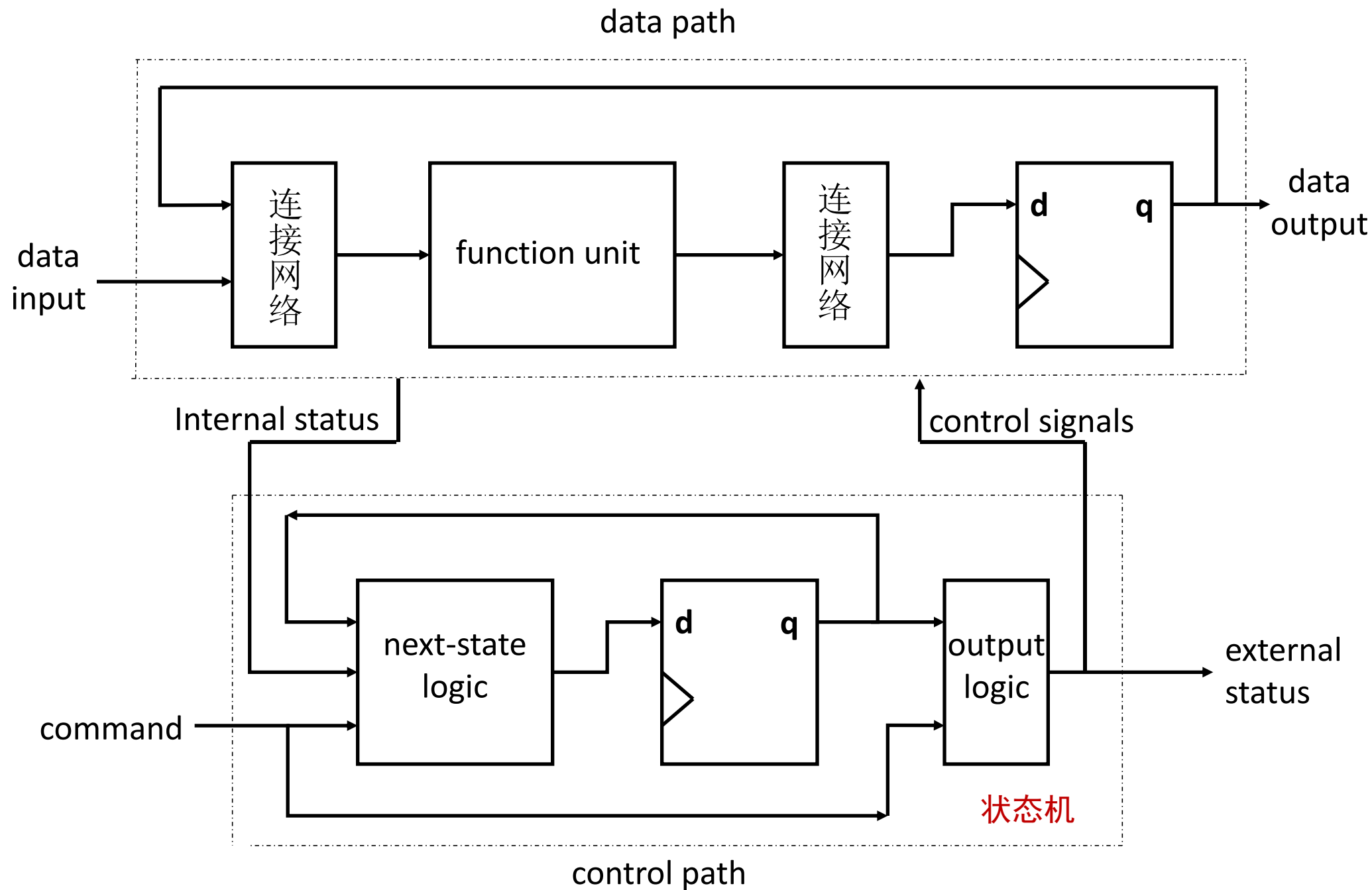

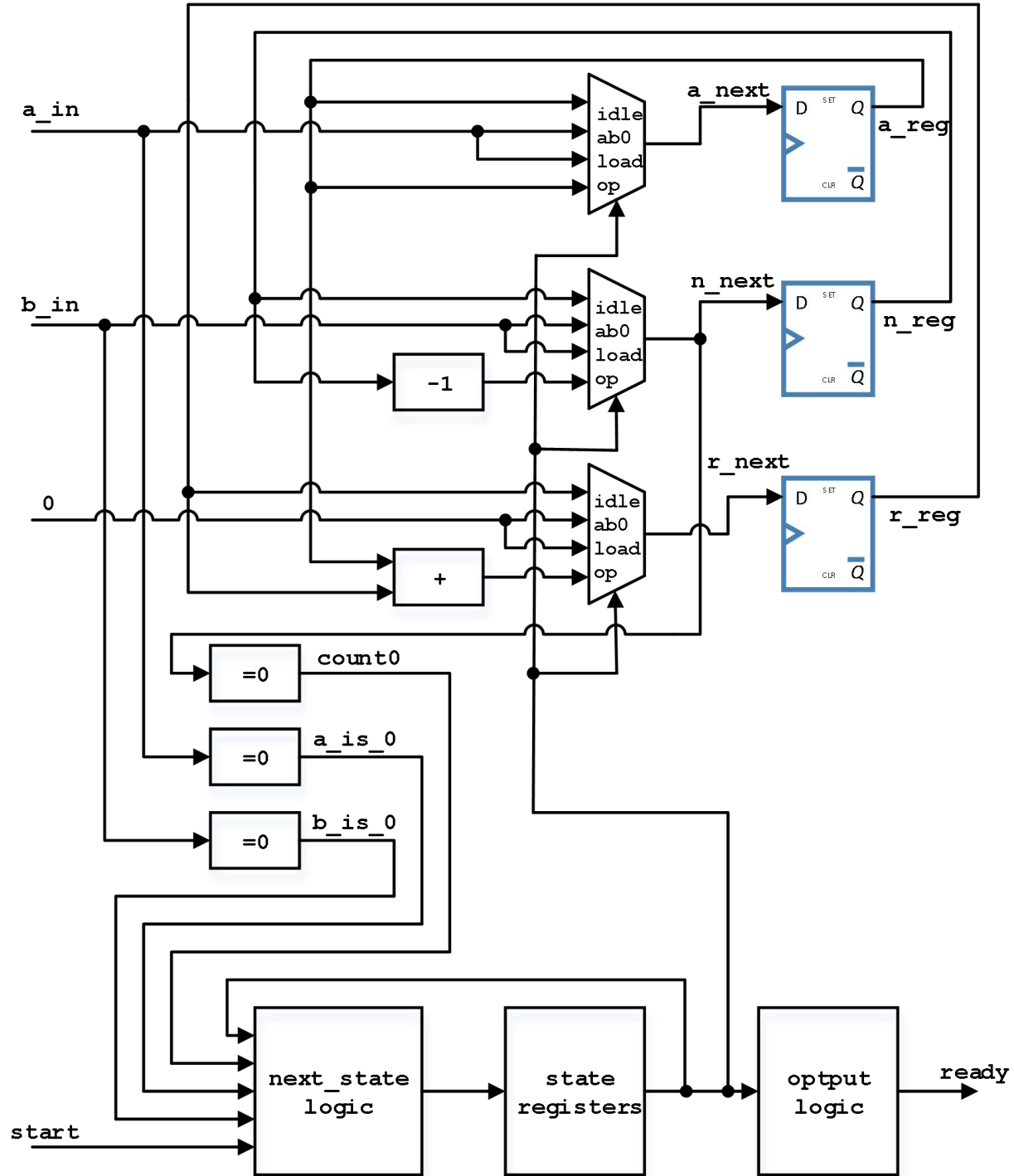

寄存器传输级设计方法

Step1: 算法和高层次状态机

Step2: 产生数据通路

Step3: 连接数据通路和控制器

Step4: 产生控制器状态机

控制通路

- 控制通路包括以下输入输出

外部命令输入

内部状态输入

控制信号输出

外部状态输出

- 时钟信号

数据通路是规则的时序电路

状态机是随机的时序电路

数据通路和控制通路通常用一个时钟信号同步

例：乘法器

输入：决定框中的信号

start: 外部命令

a_is_0, b_is_0


count_0: 内部状态

输出：

外部状态信号ready

输出控制信号control

控制通路—状态机设计

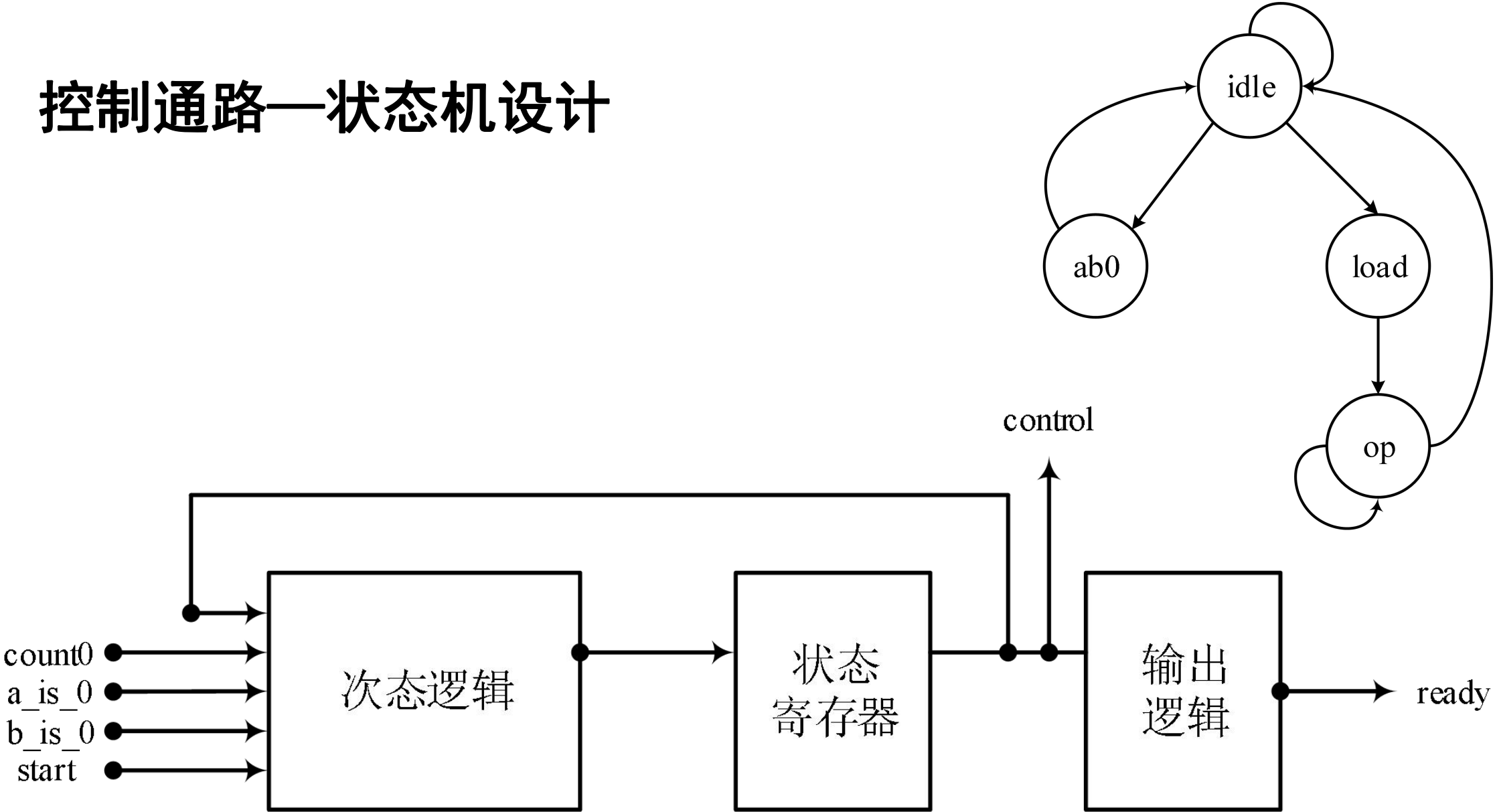


```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity sequ_mult is
port(
    clk, reset : in std_logic;
    start : in std_logic;
    a_in, b_in : in std_logic_vector(7 downto 0);
    ready : out std_logic;
    p : out std_logic_vector(15 downto 0));
end sequ_mult;
architecture rtl of sequ_mult is
    constant WIDTH : integer := 8;
    type state_type is (idle, ab0, load, op);
    signal state_reg, state_next : state_type;
    signal a_is_0, b_is_0, count_0 : unsigned(WIDTH-1 downto 0);
    signal n_reg, n_next : unsigned(WIDTH-1 downto 0);
    signal a_reg, a_next : unsigned(WIDTH-1 downto 0);
    signal r_reg, r_next : unsigned(2*WIDTH-1 downto 0);
    signal adder_out : unsigned(2*WIDTH-1 downto 0);
    signal sub_out : unsigned(WIDTH-1 downto 0);
begin
```

```
-----control path : state register-----  
    process(clk, reset)  
    begin  
        if reset = '1' then  
            state_reg <= idle;  
        elsif clk'event and clk = '1' then  
            state_reg <= state_next;  
        end if;  
    end process;  
-----control path : output logic -----  
    ready <= '1' when state_reg = idle else '0';
```

```

-----control path : next logic/output logic -----
process(state_reg, start, a_is_0, b_is_0, start, count_0)
begin
    case state_reg is
        when idle =>
            if start = '1' then
                if a_is_0 = '1' or b_is_0 = '1' then
                    state_next <= ab0;
                else
                    state_next <= load;
                end if;
            else
                state_next <= idle;
            end if;
        when ab0 => state_next <= idle;
        when load => state_next <= op;
        when op =>
            if count_0 = '1' then
                state_next <= idle;
            else
                state_next <= op;
            end if;
        end case;
    end process;
end process;

```

-----data path -----

```
process(clk, reset)
begin
```

```
    if reset = '1' then
```

```
        a_reg <= (others => '0');
```

```
        n_reg <= (others => '0');
```

```
        r_reg <= (others => '0');
```

```
    elsif clk'event and clk = '1' then
```

```
        a_reg <= a_next;
```

```
        n_reg <= n_next;
```

```
        r_reg <= r_next;
```

```
    end if;
```

```
end process;
```

-----data path: function unit-----

```
adder_out <= ("00000000" & a_reg) + r_reg;
```

```
sub_out <= n_reg - 1;
```

-----data path: routing multiplexer-----

```
process(state_reg, a_reg, n_reg, r_reg, a_in, b_in, adder_out, sub_out)
begin
```

```
    case state_reg is
```

```
        when idle =>
```

```
            a_next <= a_reg;
```

```
            n_next <= n_reg;
```

```
            r_next <= r_reg;
```

```
        when ab0 =>
```

```
            a_next <= a_in;
```

```
            n_next <= b_in;
```

```
            r_next <= (others => '0');
```

```
        when load =>
```

```
            a_next <= a_reg;
```

```
            n_next <= n_reg;
```

```
            r_next <= r_reg;
```

```
        when op =>
```

```
            a_next <= a_reg;
```

```
            n_next <= sub_out;
```

```
            r_next <= adder_out;
```

```
    end case;
```

```
end process;
```

-----data path: status-----

a_is_0 <= '1' when a_in = "00000000" else '0';

b_is_0 <= '1' when b_in = "00000000" else '0';

count_0 <= '1' when n_next = "00000000" else '0';


p <= r_reg;

end rtl;

```
if (n = 0) then{  
    go to stop;}  
else{  
    go to op;}}
```

- 软件算法：顺序的
n用计数器跟踪迭代次数
n在n=n-1语句更新


 
- ASMD图中
n <- n - 1和决定框是在同一状态
n在这个状态之后更新
判断时用的是旧的n值
条件n = 0：会多一次迭代，导致结果不正确



• 方法一：
用条件 $n = 1$ 结束循环

• 方法二：
人为插入一个等待状态 **wait**
条件判断时 n 已经更新
每次迭代引入一个时钟周期
性能下降

• 方法三：
用 n 的下一次值判断

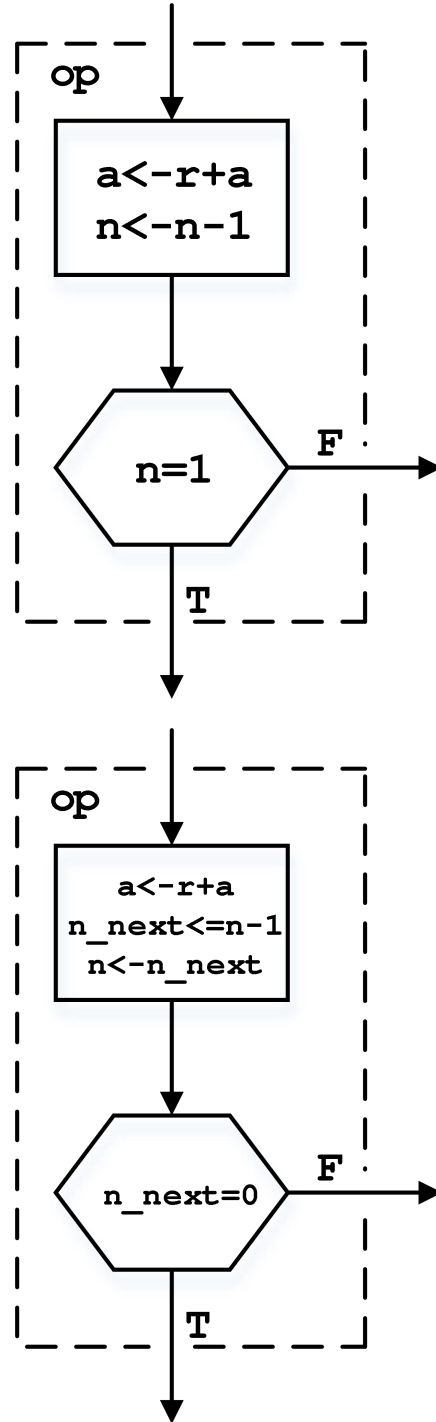 

寄存器传输设计方法的关键如何得到是算法高效的ASMD图

在决定框中的布尔表达式中使用寄存器

上面的例子中：状态信号

a_is_0

b_is_0

count_0

另一种方法：

用寄存器和输入信号直接表示布尔条件

a_in, b_in


乘法器的改进

- 前面的设计

- 在idle状态，在决定框中用到a_in
b_in
- 在ab0或load状态把a_in、b_in
加载到寄存器
- 实际加载是在两个时钟周期之后

- 优化

- 对start、a_in、b_in同时采样

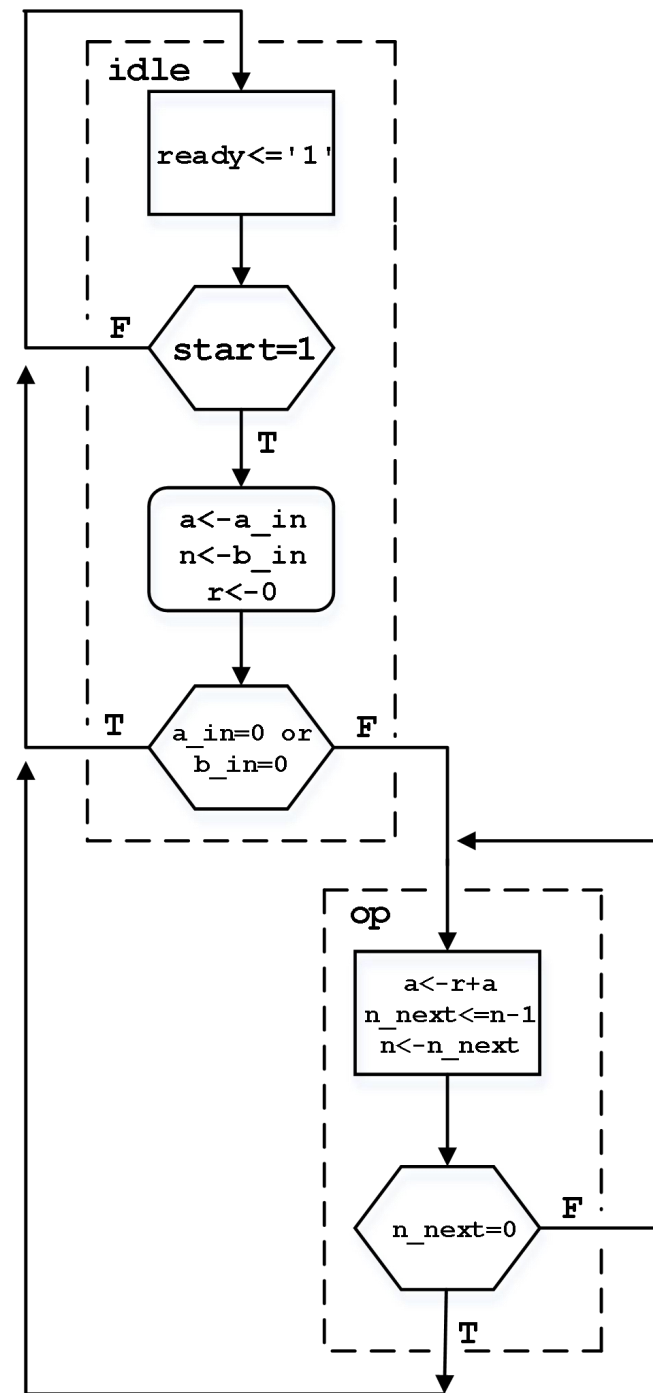

architecture rtl2 of sequ_mult is

 constant WIDTH : integer := 8;

 type state_type is (idle, op);

 signal state_reg, state_next : state_type;

 signal n_reg, n_next : unsigned(WIDTH-1 downto 0);

 signal a_reg, a_next : unsigned(WIDTH-1 downto 0);

 signal r_reg, r_next : unsigned(2*WIDTH-1 downto 0);

begin

-----state and data register-----

 process(clk, reset)

 begin

 if reset = '1' then

 state_reg <= idle;

 a_reg <= (others => '0');

 n_reg <= (others => '0');

 r_reg <= (others => '0');

 elsif clk'event and clk = '1' then

 state_reg <= state_next;

 a_reg <= a_next;

 n_reg <= n_next;

 r_reg <= r_next;

 end if;

 end process;

-----combinational logic-----

process(start, state_reg, a_reg, n_reg, r_reg, a_in, b_in)

begin

 a_next <= a_reg; n_next <= n_reg;

 r_next <= r_reg; ready <= '0';

 case state_reg is

 when idle =>

 if start = '1' then

 a_next <= a_in; n_next <= b_in;

 r_next <= (others => '0');

 if a_in = "00000000" or b_in = "00000000" then

 state_next <= idle;

 else

 state_next <= op;

 end if;

 end if;

 ready <= '1';

 when op =>

 n_next <= n_reg - 1;

 r_next <= r_reg + ("00000000" & a_reg);

 if n_next = "00000000" then

 state_next <= idle;

 else

 state_next <= op;

 end if;

 end case;

end process;

r <= r_reg;

end rtl2;